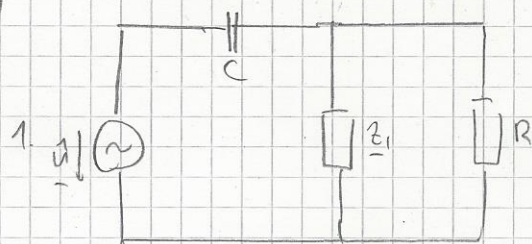



$$\hat{u} = \hat{u} \cdot e^{j\varphi}$$

a)




$$Z_1 = R_w + j\omega L$$
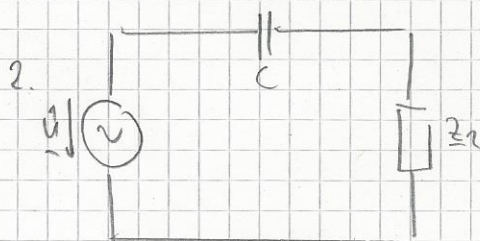
$$X (= 1,241 \Omega \cdot e^{j14,07^\circ})$$



$$Z_2 = Z_1 // R = \frac{(R_w + j\omega L) \cdot R}{R + R_w + j\omega L}$$
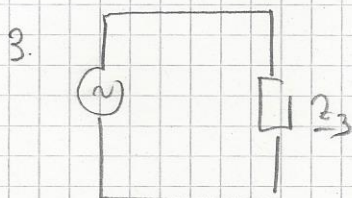
$$= \frac{RR_w + j\omega RL}{R + R_w + j\omega L} \quad Y (= 883,562 \text{ mS} \cdot e^{j10,39^\circ})$$



$$Z_3 = \frac{1}{j\omega C} + \frac{RR_w + j\omega RL}{R + R_w + j\omega L}$$

$$= \frac{R + R_w + j\omega L + j\omega C (RR_w + j\omega RL)}{j\omega C (R + R_w + j\omega L)}$$

$$= \frac{R + R_w + j\omega L + j\omega RR_w C - \omega^2 RLC}{j\omega RC + j\omega R_w C - \omega^2 LC}$$

$$= \frac{R + R_w - \omega^2 RLC + j\omega (L + RR_w C)}{-\omega^2 LC + j\omega (RC + R_w C)} \quad Z_L (= 991,47 \text{ mS} \cdot e^{-j28,77^\circ})$$

$$\hat{u}_R = \hat{u} \cdot \frac{RR_w + j\omega RL}{R + R_w + j\omega L} \cdot \frac{1}{j\omega C + \frac{RR_w + j\omega RL}{R + R_w + j\omega L}}$$

$$= \hat{u} \cdot \frac{RR_w + j\omega RL}{R + R_w + j\omega L + (RR_w + j\omega RL)j\omega C}$$

$$= \hat{u} \cdot \frac{(RR_w + j\omega RL)j\omega C}{R + R_w + j\omega L + j\omega RR_w C - \omega^2 RLC} = \hat{u} \cdot \frac{-\omega^2 RLC + j\omega RR_w C}{R + R_w + \omega^2 RLC + j\omega (R_w C + L)}$$

$$\underline{\underline{Z_{in}}} = \frac{R + R_w - \omega^2 RLC + j\omega(L + RR_w C)}{-\omega^2 LC + j\omega(RC + R_w C)}$$

$$\underline{\underline{U_R}} = \underline{\underline{U}} \cdot \frac{-\omega^2 RLC + j\omega R R_w C}{R + R_w - \omega^2 RLC + j\omega(R R_w C + L)}$$

b) $R = 3\Omega$, $C = 5\text{mF}$, $L = 1\text{mH}$, $\overset{s}{R_w} = 1,2\Omega$, $\omega = 2\pi 50 \text{ Hz}$
 $\underline{\underline{U}} = 5\text{V} \cdot e^{j100}$

$$\underline{\underline{U_R}} = 4,46\text{V} \cdot e^{j39,16^\circ}$$

$$\underline{\underline{I}} = \frac{\underline{\underline{U}}}{\underline{\underline{Z_{in}}}} = 5,04\text{A} \cdot e^{j28,79^\circ}$$

c) $\underline{\underline{I_L}} = \frac{\underline{\underline{U_R}}}{\underline{\underline{Z_1}}} = 3,59\text{A} \cdot e^{j14,67^\circ}$

$$\underline{\underline{I_R}} = \frac{\underline{\underline{U_R}}}{R} = 1,485\text{A} \cdot e^{j39,16^\circ}$$

$$\underline{\underline{U_C}} = \underline{\underline{I}} \cdot \frac{j\omega C}{\frac{1}{j\omega C} + \underline{\underline{Z_2}}} = 3,21\text{V} \cdot e^{-j3,43^\circ}$$

$$\underline{\underline{U_L}} = j\omega L \cdot \underline{\underline{I_L}} = 1,13\text{V} \cdot e^{j14,49^\circ}$$

d) $\omega_0 = \frac{1}{\sqrt{LC}} = 447,21 \frac{1}{\text{s}} \Rightarrow \underline{\underline{f_0 = 71,2\text{Hz}}}$

$$\text{Im}(\underline{\underline{I}}) = 0$$

$$5,04\text{A} \cdot e^{j\omega} = 0 \Rightarrow$$