

3a i) $v_d(t) = 0$ $i_+(t) = 0$

ii) $v_x(t) = i_{in}(t) R_3$ $v_{R1}(t) = v_x(t)$

ϕ_1 geschl. $\rightarrow v_{out}(t) = v_{R1}(t)$

ϕ_2 offen $\rightarrow i_{R2}(t) = i_{R1}(t) = \frac{v_{R1}(t)}{R_1} = i_{in}(t) \frac{R_3}{R_1}$

$$v_{out}(t) = v_{R2}(t) + v_{R1}(t) = i_{in}(t) \left(\frac{R_2 R_3}{R_1} + R_3 \right)$$

iii) (Nicht-invertierender) Verstärker mit zwei verschiedenen Verstärkungsfaktoren


3b i) $Z_{tot} = R_1 + R_2 + j\omega 2L$

ii) $\underline{v}_{L2} = \underline{v}_s \frac{Z_{L1} \parallel L_2}{Z_{tot}} = \frac{A}{\sqrt{2}} e^{j\phi_0} \frac{j\omega 2L}{R_1 + R_2 + j\omega 2L}$

iii) $\underline{I}_{L1} = \frac{\underline{v}_{L1}}{Z_{L1}}$

$$\angle(\underline{I}_{L1}) = \phi_0 - \arctan\left(\frac{\omega 2L}{R_1 + R_2}\right)$$

$$|\underline{I}_{L1}| = \frac{A}{3\sqrt{2}} \frac{1}{\sqrt{(R_1 + R_2)^2 + (\omega 2L)^2}}$$

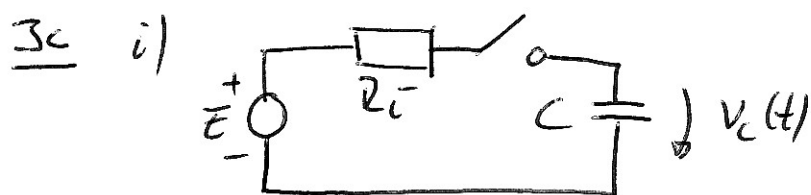


$$R_i = 300 \Omega$$

$$E = I R_i = 1,8 V$$

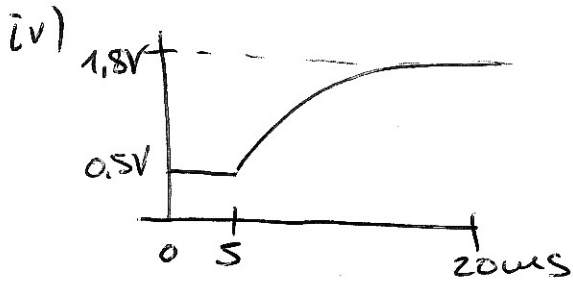ii) $v_C(t_0+) = \frac{Q_0}{C} = 500 mV$

$$i_C(t_0+) = \frac{E - v_C(t_0+)}{R_i + R_{sw,on}} = 1,432 mA$$

$$iii) V_C(t_0 \rightarrow \infty) = E = 1,8V$$



$$t_0 = 5ms$$

$$V_C(t_0) = 0,5V$$

$$V_C(t_0 \rightarrow \infty) = 1,8V$$

$$v) \tau = (R_1 + R_{sw,on}) C = 2,724 \mu s$$

$$V_C(t) = E - (E - V_C(t_0)) e^{-\frac{t-t_0}{\tau}}$$

$$V_C 95\% = 0,95 E = V_C(t_{95})$$

$$\rightarrow t_{95} = 12,27 \mu s$$