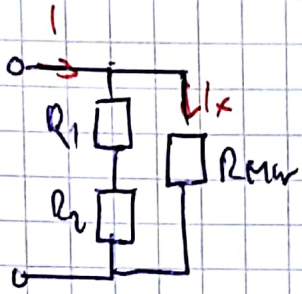


$$a) P_{\max} = 8 \text{ mW} = I_{\text{NW}}^2 \cdot R_{\text{NW}} \Rightarrow I_{\text{NW}} = \sqrt{\frac{P_{\max}}{R_{\text{NW}}}} = \underline{\underline{8,944 \text{ mA}}}$$

MB1:




$$I_x = I \cdot \frac{R_1 + R_2}{R_1 + R_2 + R_{\text{NW}}}$$

$$\Rightarrow 8,944 \text{ mA} = 500 \text{ mA} \cdot \frac{R_1 + R_2}{R_1 + R_2 + 100 \Omega}$$

$$\Rightarrow R_1 + R_2 = 1,821 \Omega$$

MB2:

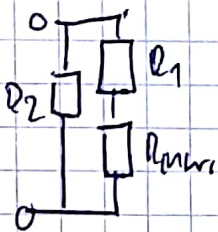

$$I_x = I \cdot \frac{R_2}{R_1 + R_2 + 100 \Omega} = I \cdot \frac{R_2}{101,821 \Omega}$$

$$\Rightarrow R_2 = \frac{8,944 \text{ mA}}{1500 \text{ mA}} \cdot 101,821 \Omega = \underline{\underline{0,6 \Omega}}$$

$$\underline{\underline{R_1 = 1,214 \Omega}}$$

Rundungsfehler
($Z \neq 1,812 \Omega$)

$$P_{1, \max}: I_{2, \max} = 1500 \text{ mA} - 8,944 \text{ mA} = 1491,06 \text{ mA}$$

$$\Rightarrow P_{1, \max} = (1491,06 \text{ mA})^2 \cdot R_1 = \underline{\underline{2,7 \text{ W}}}$$

$$P_{2, \max} = I^2 R_2$$

$$b) \underline{P_{2,max}} = I_{2,max}^2 \cdot R_2 = (1.5 A - 8.944 mA)^2 \cdot 0.6 \Omega = \underline{\underline{1.334 W}}$$

$$P_{1,max} = I_{1,max}^2 \cdot R_1$$

$$I_{1,max} : \max \{ 8.944 mA, 0.5 A - 8.944 mA \} = 0.5 A - 8.944 mA$$

$$\Rightarrow \underline{P_{1,max}} = (0.5 A - 8.944 mA)^2 \cdot 1.214 \Omega = \underline{\underline{0.293 W}}$$

$$U_{in} = I_{in} \cdot R_{in} = U_n$$

$$R_{in}(MB1) = (R_1 + R_2 \parallel R_{nw}) = \underline{\underline{1.788 \Omega}}$$

$$R_{in}(MB2) = (R_2 \parallel R_{nw} + R_1) = \underline{\underline{0.596 \Omega}}$$

$$\Rightarrow U_{in}(MB1) = 0.5 \cdot 1.788 = 0.894$$

$$U_{in}(MB2) = 1.5 \cdot 0.596 = 0.894$$

$$\underline{\underline{U_{max} = 0.894 V}}$$