
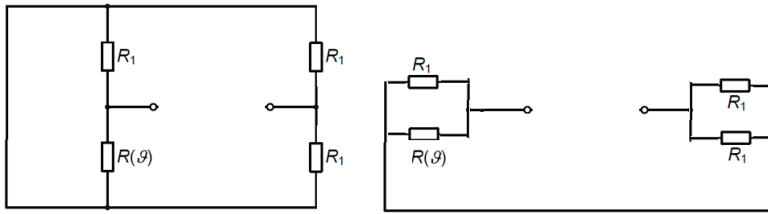


Aufgabe 1 - Folien

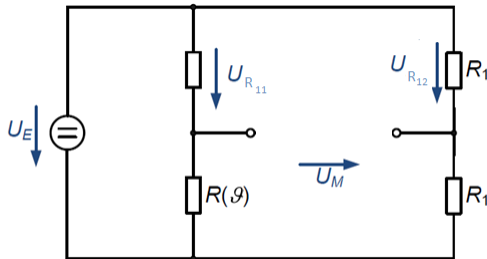


$$R_i = (R_1 || R_1) + (R_1 || R(\vartheta)) = \frac{R_1}{2} + \frac{R_1 \cdot R(\vartheta)}{R_1 + R(\vartheta)}$$

Für die Spannung U_M gilt:



$$U_M = -U_{R_{11}} + U_{R_{12}}$$

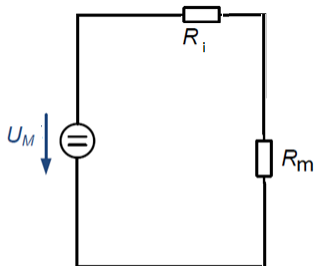Aus Spannungsteilerregel folgt: $U_{R_{11}} = U_E \cdot \frac{R_1}{R_1 + R(\vartheta)}$ und $U_{R_{12}} = \frac{U_E}{2}$
 $\rightarrow U_M = U_E \cdot \left(\frac{1}{2} - \frac{R_1}{R_1 + R(\vartheta)} \right)$



b)

$$R(30) = 2k\Omega \rightarrow U_M = U_E \cdot \left(\frac{1}{2} - \frac{1}{3} \right) = 4V$$

$$R_i = 500\Omega + \frac{2000}{3} = 1166.7\Omega$$

$$\text{Spannung über } R_m : \text{Spannungsteiler} \rightarrow U_M \frac{R(m)}{R_m + R_i} = 3.995V$$